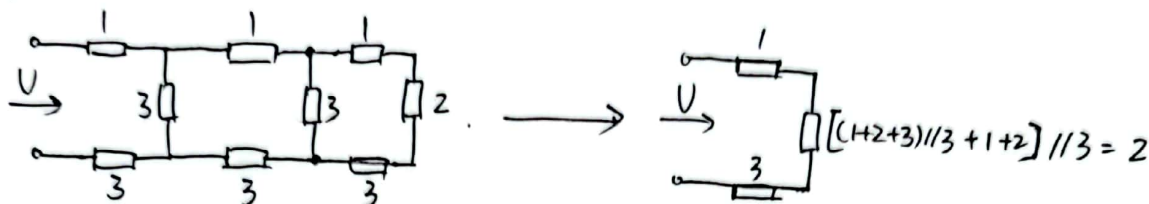


$$\therefore U = -I - 25$$


2.



$$\therefore U_R = \frac{2}{1+2+3} \times \frac{2}{1+2+3} \times \frac{2}{1+2+3} U_s$$

$$= \left(\frac{1}{3}\right)^3 U_s$$

$$= e^{-t} \sinh 2t \text{ V}$$

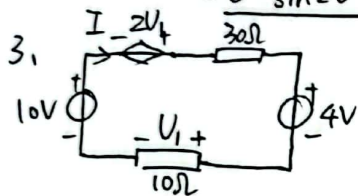


回路KVL有: $\begin{cases} U_1 = 10I \\ 10 + 2V_1 = 30I + 4 + U_1 \end{cases}$

$$\therefore I = 0.3 \text{ A}$$

$$\therefore P_S = U_S I = 10 \times 0.3 = 3 \text{ W}$$

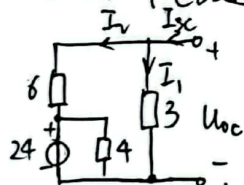4. 对除R外电路进行戴维宁等效: $\begin{cases} U_{oc} = 6I_2 + 24 \\ U_{oc} = 3I_1 \end{cases}$



$$\therefore U_{oc} = (2I_{sc} + 8) \text{ V}$$

$$\text{即: } \begin{cases} U_{oc} = 8 \text{ V} \\ R_{eq} = 2 \Omega \end{cases}$$

$$\therefore R = 2 \Omega \text{ 时, } P = P_{\max}$$

$$\text{此时 } P_{\max} = \frac{U_{oc}^2}{4R} = 8 \text{ W}$$

5. 对该电路书写节点电压方程: $\begin{cases} 5U_{n1} - 3U_{n2} = 2 \\ -3U_{n1} + 7U_{n2} = 9 \text{ V} \\ U_{n1} - U_{n2} = -U \end{cases}$ 与原式对比.

$$\therefore g = 2 \text{ S}$$

$$6. \text{ 令 } \dot{I}_{A1} = 5 \angle 0^\circ \text{ A} \quad \therefore \dot{I}_{A2} = 20 \angle 90^\circ \text{ A} \quad \dot{I}_{A3} = 25 \angle 90^\circ \text{ A}$$

$$\text{即: } U = \dot{I}_{A1} R = \omega L \dot{I}_{A2} = \frac{1}{\omega C} \dot{I}_{A3}$$

$$\text{若 } \omega = 2\omega_0 \text{ 有: } U = \dot{I}_{A1} R = 2\omega_0 L \dot{I}_{A2} = \frac{1}{2\omega_0 C} \dot{I}_{A3}$$

$$\therefore \dot{I}_{A2}' = 10 \angle 90^\circ \text{ A}, \quad \dot{I}_{A3}' = 50 \angle 90^\circ \text{ A}$$

$$\therefore |\dot{I}_A| = |\dot{I}_{A1} + \dot{I}_{A2}' + \dot{I}_{A3}'| = \sqrt{5^2 + (50-10)^2} = \sqrt{1625} \text{ A} = 5\sqrt{65} \text{ A} \approx 40.3 \text{ A}$$




7. $\dot{U} = -5 - j5 \text{ V} = 5\sqrt{2} \angle -135^\circ \text{ V}$.

$\therefore u(t) = \frac{10 \cos(10t - 135^\circ) \text{ V}}{\text{or}}$ (更优)


$u(t) = 10 \sin(10t - 135^\circ) \text{ V}$

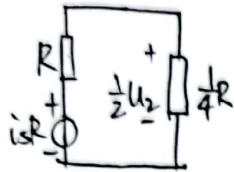8. 变压器等效有: 即: $\frac{1}{2}u_2 = \frac{1}{5}i_5 R$



即: $u_2 = \frac{2}{5}i_5 R$

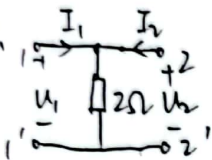
9. $\begin{cases} u_1 = 2I_1 + 2I_2 \\ u_2 = 2I_1 + 2I_2 \end{cases}$



$\therefore Z_{11} = 2 \Omega$


PS: $Z = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \Rightarrow \begin{pmatrix} u_1 \\ u_2 \end{pmatrix} = Z \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$

10. 断开开关后: 对 L 有等效电路转换:

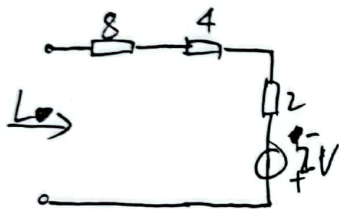

$\therefore R_{eq} = 14 \Omega$

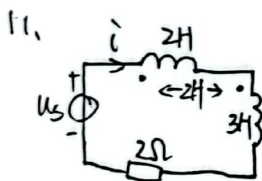$\therefore \tau = \frac{L}{R_{eq}} = \frac{1}{14} \text{ s}$



$i(0^-) = 0 \text{ A}$

$i(\infty) = \frac{u_s}{R} = 0.5 \text{ A}$

$L_{eq} = L_1 + L_2 + 2M = 2 + 3 + 2 \times 2 = 9 \text{ H}$

$\tau = \frac{L}{R_{eq}} = \frac{9}{2} \text{ s}$

$\therefore i(t) = 0.5(1 - e^{-\frac{2}{9}t}) \text{ A}$


$\therefore i(1\text{s}) = (0.5 - 0.5e^{-\frac{2}{9}}) \text{ A}$

12. 状态1时: $u_c(0) = 0 \text{ V}$, $u_c(\infty) = 2 \text{ V}$. $u_s(t) = 4\varepsilon(t) \text{ V}$. $\tau = 1 \text{ s}$.

状态2时: $u_s(t) = 8\varepsilon(t) \text{ V} \Rightarrow u_c(\infty) = 4 \text{ V}$.

$\therefore u_c(t) = (4 - e^{-t}) \text{ V}$

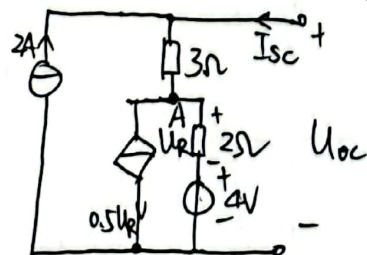二、对除 R_L 以外其余进行戴维宁等效: $\begin{cases} u_{oc} = 3(2 + I_{sc}) + u_R + 4 \\ 2 + I_{sc} = 0.5u_R + \frac{u_R}{2} \end{cases}$ (A 结点 KOL)



$\therefore u_{oc} = 4I_{sc} + 12$


即: $\begin{cases} R_{eq} = 4 \Omega \\ u_{oc} = 12 \text{ V} \end{cases}$

$\therefore P_{R_L} = \left(\frac{u_{oc}}{R_{eq} + R} \right)^2 R = 9 \text{ W}$



三. $u_c(0_-) = 5V$.

S 闭合后, 有等效电路




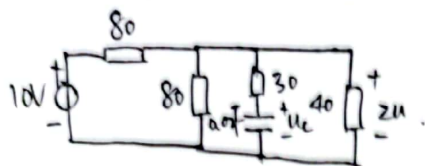


$\therefore T = Req C = 1s$

$u_c(0_+) = 2.5V$

$\therefore u_c(t) = 2.5e^{-t} V$

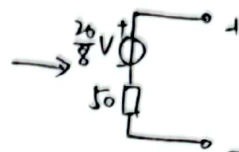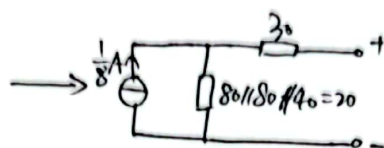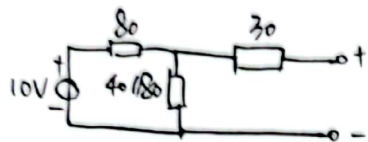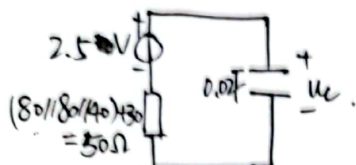$\therefore u(t) = \frac{u_c(t)}{2} = 1.25(1+e^{-t})V$




IV. (1) $u_s = \sqrt{12^2 + 15^2 + 16^2} = 25V$

(2) C, L, 并联谐振频率: $\omega = \sqrt{\frac{1}{LC}} = 10^3 \text{ rad/s}$.

$\therefore u_R = 12 + 16\sqrt{2}\cos(2\omega t)$ (ω 时发生并联谐振)

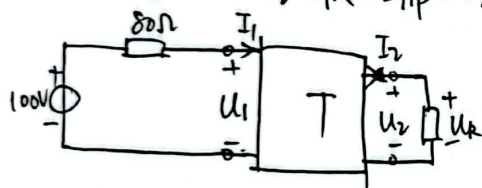(3) $P = \frac{u_R^2}{R} = 12^2 + (\frac{16\sqrt{2}}{\sqrt{2}})^2 = 400W$.

五. 对于 T_1, T_2 级联二端口, 有: $T = T_1 T_2 = \begin{pmatrix} 1 & 10 \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ 20.5 & 1 \end{pmatrix}$




即: $\begin{cases} u_1 = 1.5u_2 + 10I_2 \\ I_1 = 0.05u_2 + I_2 \end{cases}$

故有: $\begin{cases} I_1 = 1A \\ I_2 = 0.5A \\ u_R = 20I_2 = 10V \end{cases}$


$\therefore \begin{cases} u_2 = u_R \\ u_R = 20I_2 \\ 100 = 80I_1 + u_1 \end{cases}$

(注意 I_2 方向)

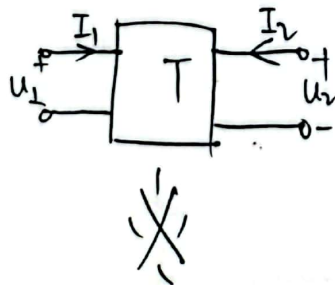PS: $\begin{pmatrix} u_1 \\ I_1 \end{pmatrix} = T \begin{pmatrix} u_2 \\ -I_2 \end{pmatrix}$



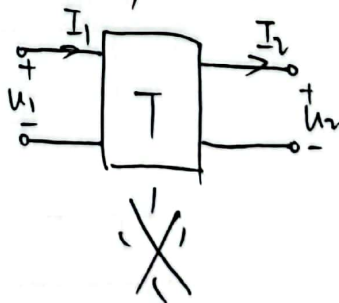$\begin{pmatrix} u_1 \\ I_1 \end{pmatrix} = T \begin{pmatrix} u_2 \\ I_2 \end{pmatrix}$



扫描全能王 创建