
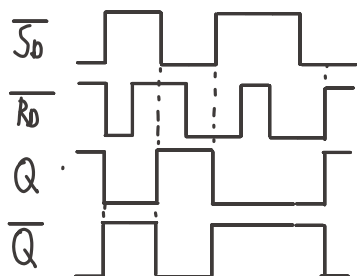


# 数字电子技术第七次作业


44解 波形图如下

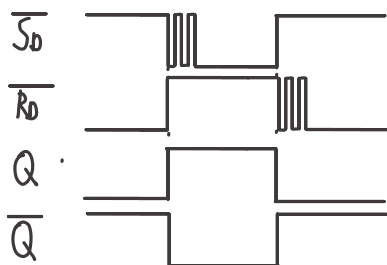


46解 波形图如下




47解 设CP=1时进行状态更新

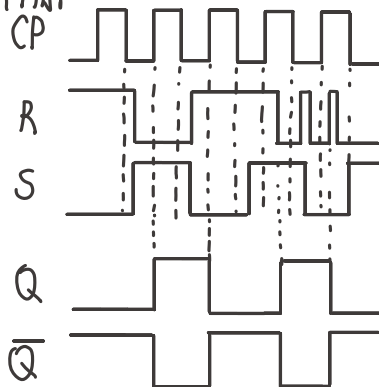


49解

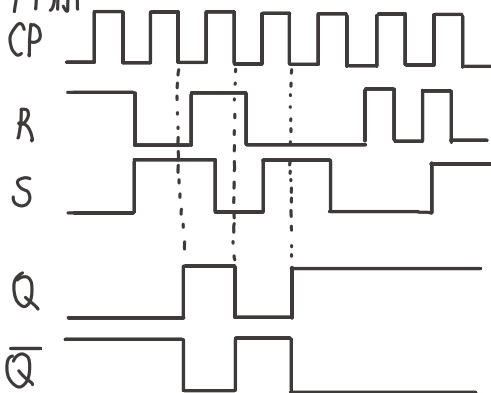


4.10解

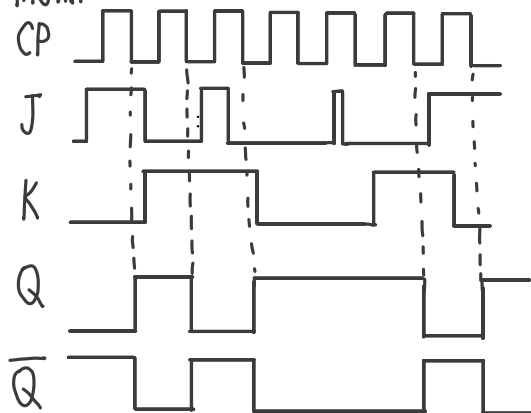


4.11 解

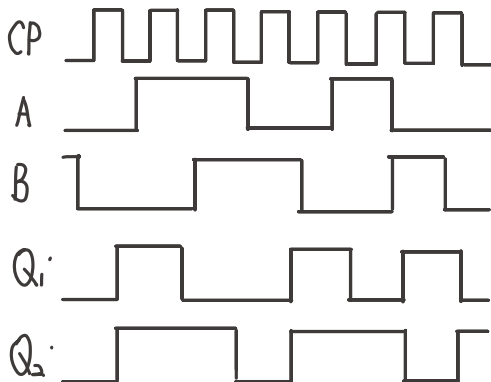


4.12 解:

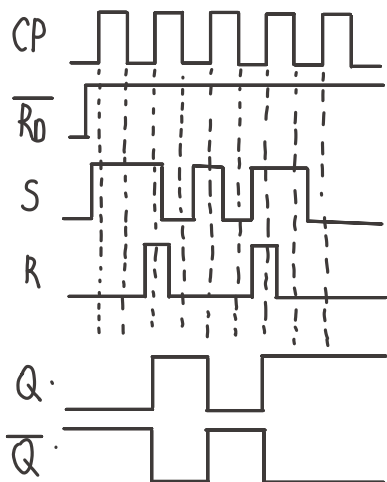

4.13 解:

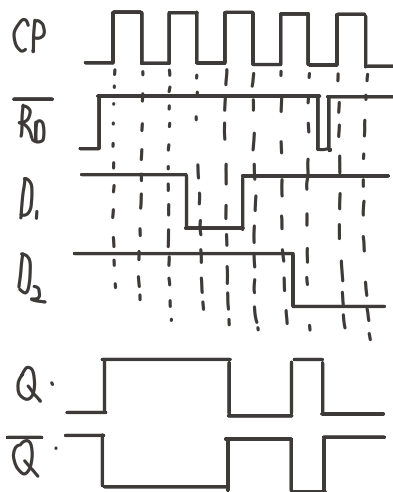

4/4 解

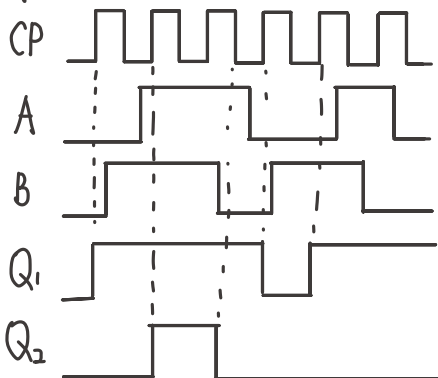

4/5 解

