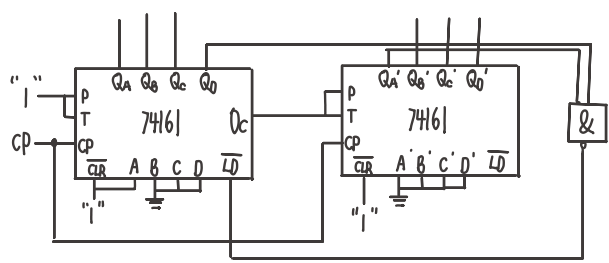


数字电子技术第九次作业

516 使用两片 74161 芯片级联，分别使用 $Q_0' \sim Q_A'$ ， $Q_0 \sim Q_A$ 生成从高位到低位的二进制数：
 $\overline{LD} = \overline{Q_A' Q_0}$ ，得电路图如下



517 解 容易发现该电路由两块同步置位的 74161 芯片串联而成，当代表高 4 位的 74161 芯片输出进位信号时两块芯片被同时置数，易得预置值应该为十进制数 $256-M$ 的二进制原码表示

$\therefore M=100$ 时， $I_7 \sim I_0$ 预置值为 $[156]_{10} = [10011100]_2$

$M=250$ 时， $I_7 \sim I_0$ 预置值为 $[56]_{10} = [00111000]_2$


当 $I_7 \sim I_0 = 01101000$ $M = 256 - [01101000]_2 = 152$

518 解 序列信号为 1101000101，故将 74161 改造为模 10 计数器， $Q_0 \sim Q_A = 1001$ ，同步预置信号激活多路选择器使用 CC4512 芯片

电路状态表如下

Q_0	Q_1	Q_2	Q_3	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1

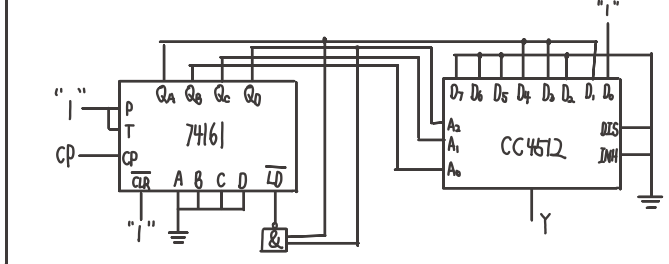
\therefore 令 $A_0 = Q_0$ $A_1 = Q_1$ $A_2 = Q_2$ $\overline{LD} = \overline{Q_A Q_0}$
 $D_0 = 1$ $D_2 = 0$ $D_1 = D_3 = D_4 = Q_A$ $D_5 = D_6 = D_7 = 0$
 给出如下电路图



519 解 使用2片74LS194 芯片级联实现模10位移计数器(生成格雷码)

使 Q_0' 和 $Q_3 \sim Q_6$ 作为计数输出端, 数码映射如下

状态	$Q_6' Q_3 Q_2 Q_1 Q_0$ 位表示	电路图如下(假设初态为00000)
0	0 0 0 0 0	
1	0 0 0 0 1	
2	0 0 0 1 1	
3	0 0 1 1 1	
4	0 1 1 1 1	
5	1 1 1 1 1	
6	1 1 1 1 0	
7	1 1 1 0 0	
8	1 1 0 0 0	
9	1 0 0 0 0	

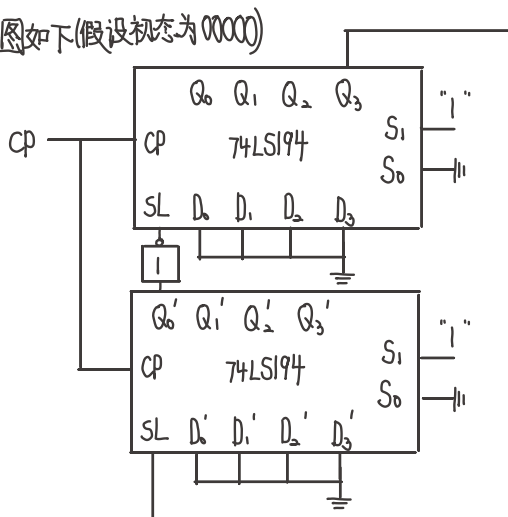

(1-8)

520 解 使 74161 芯片构建 8 计数器和 CC4512 数据选择器生成序列码

状态表如下


$Q_6 Q_5 Q_4 Q_3 Q_2 Q_1 Q_0$	Y
0 0 0 0 1 0 0	0
0 0 0 1 0 0 0	0
0 0 1 1 1 0 0	0
0 1 0 0 0 1 1	1
0 1 0 1 1 1 1	1
0 1 1 0 1 1 1	1
0 1 1 1 0 1 1	1
1 0 0 0 0 1 1	0

$$\therefore \text{令 } A_2 = Q_6, A_1 = Q_5, A_0 = Q_4$$

$$\therefore D_0 = D_1 = 0, D_2 = D_3 = 1, \overline{LD} = \overline{Q_0}$$

$$D_4 = \overline{Q_6}, D_5 = D_6 = D_7 = 0$$

得电路图如下

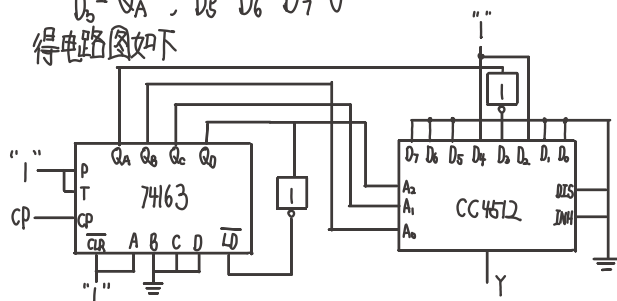

5.21 解: 容易得到电路图需要4个JK触发器 $Q_3 - Q_0$ 代表BCD码的四位

状态转移表如下

Q_3^n	Q_2^n	Q_1^n	Q_0^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}								
0	0	0	0	0	0	0	1		0	0	0	1	0	0	1
0	0	0	1	0	0	1	0		0	0	1	0	0	0	0
0	0	1	0	0	0	1	1		0	1	0	0	0	0	0
0	0	1	1	0	1	0	0		0	1	1	0	0	0	0
0	1	0	0	0	1	0	1		1	0	0	0	0	0	0
0	1	0	1	0	1	1	0		1	0	1	0	0	0	0
0	1	1	0	0	1	1	1		1	1	0	0	0	0	0
0	1	1	1	1	0	0	0		1	1	1	0	0	0	0

用卡诺图化简得


$$Q_3^{n+1} = Q_3^n \bar{Q}_0^n + \bar{Q}_3^n Q_2^n Q_1^n Q_0^n, \text{ 故 } J_3 = Q_2^n Q_1^n Q_0^n, K_3 = Q_0^n$$

$$Q_2^{n+1} = \bar{Q}_2^n \quad Q_1^n Q_0^n + Q_2^n (\bar{Q}_1^n + Q_1^n \bar{Q}_0^n), \text{ 故 } J_2 = Q_1^n Q_0^n, K_2 = Q_1^n Q_0^n$$

$$Q_1^{n+1} = \bar{Q}_1^n \bar{Q}_3^n Q_0^n + Q_1^n \bar{Q}_0^n, \text{ 故 } J_1 = \bar{Q}_3^n Q_0^n, K_1 = \bar{Q}_0^n$$

$$Q_0^{n+1} = \bar{Q}_0^n, \text{ 故 } J_0 = 1, K_0 = 1 \quad Z = Q_3^n Q_0^n \text{ (进位标志)}$$

电路图如下

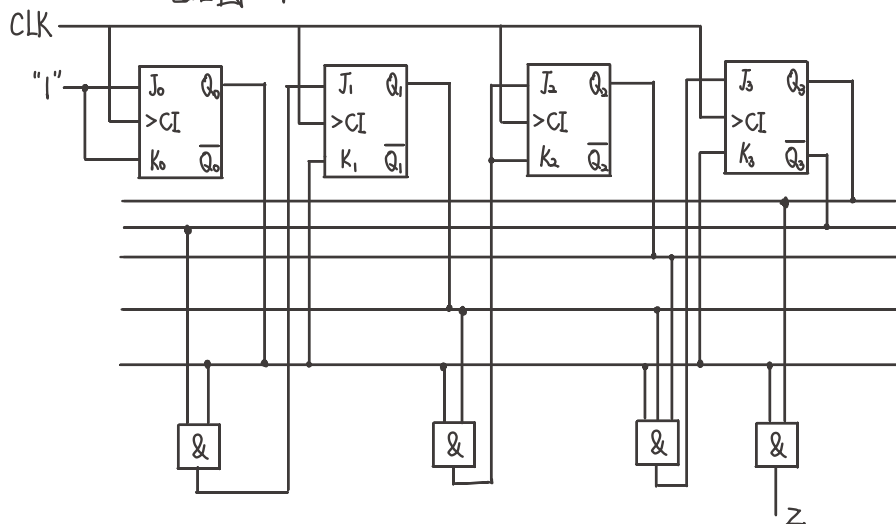

5.22 解: 其原始状态表如下

$S^m/Z^n \backslash X$	0	1
S^n		
S0	S0/0	S1/0
S1	S2/0	S3/0
S2	S4/0	S5/1
S3	S6/1	S7/0
S4	S8/0	S9/0
S5	SA/0	SB/0
S6	SC/0	SD/1
S7	SE/0	SF/0

续

$S^m/Z^n \backslash X$	0	1
S^n		
S8	S0/0	S1/0
S9	S2/0	S3/0
SA	S4/0	S5/1
SB	S6/1	S7/0
SC	S8/0	S9/0
SD	SA/0	SB/0
SE	SC/1	SD/1
SF	SE/0	SF/0

5.23 (a) 作隐含表如下

B	x								
C	x	x							
D	x	x	x						
E	x	x	x	✓					
F	✓	x	x	x	x				
G	x	x	✓	x	x	x			
H	x	✓	x	x	x	x	x		
I	x	x	x	x	x	x	x	x	
A	B	C	D	E	F	G	H		

简化后状态表

	0	1
A	A/0	C/1
B	B/1	C/0
C	B/0	A/0
D	C/1	D/0
I	B/0	D/0


(b) 作隐含表如下

B	x								
C	x	✓							
D	x	x	x						
E	x	x	x	x					
F	✓	x	x	x	x				
G	x	x	x	x	x	x			
H	x	✓	✓	x	x	x	x		
A	B	C	D	E	F	G			

简化后状态表

	00	01	10	11
A	D/0	D/0	A/0	A/0
B	B/1	D/0	A/0	E/1
D	D/0	B/0	A/0	E/1
E	B/1	A/0	A/0	E/1
G	G/0	G/0	A/0	A/0

5.25 解 易得至少需要4个触发器，状态图如下

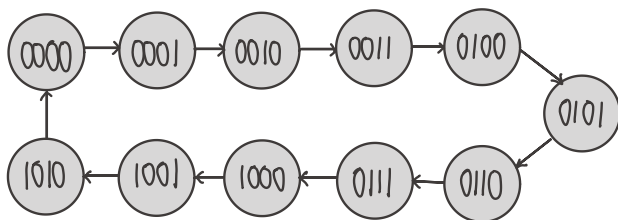

状态表如下

Q_3^n	Q_2^n	Q_1^n	Q_0^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1

续表

0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	0	0	0	0

$$D_0 = \overline{Q_1^n} \overline{Q_0^n} + \overline{Q_3^n} \overline{Q_0^n} \quad Z = Q_3^n Q_1^n \quad (\text{进位输出})$$

$$D_1 = \overline{Q_1^n} \overline{Q_0^n} + \overline{Q_3^n} Q_1^n \overline{Q_0^n}$$

$$D_2 = Q_3^n \overline{Q_1^n} + \overline{Q_3^n} Q_1^n Q_0^n + Q_2^n \overline{Q_0^n}$$

$$D_3 = Q_3^n \overline{Q_1^n} + Q_2^n Q_1^n Q_0^n$$

