

# 数字电子技术

3 9 ABCD表示四个开关的开闭状态, Y表示灯的亮灭

写出真值表

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1


续表

1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

∴ 写出逻辑表达式

$$Y = \sum (m_1, m_2, m_4, m_7, m_8, m_{11}, m_{13}, m_{14})$$

可以使用数据选择器构建电路

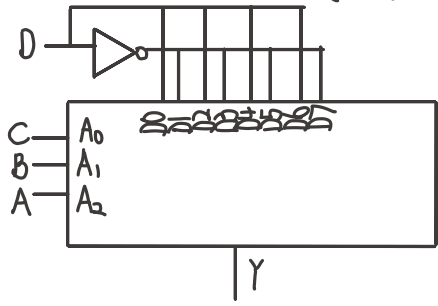

3 10 写出真值表


8421 BCD码	循环码	余3码	2421 码
$B_3 B_2 B_1 B_0$	$X_3 X_2 X_1 X_0$	$Y_3 Y_2 Y_1 Y_0$	$E_3 E_2 E_1 E_0$
0 0 0 0	0 0 0 0	0 0 1 1	0 0 0 0
0 0 0 1	0 0 0 1	0 1 0 0	0 0 0 1
0 0 1 0	0 0 1 1	0 1 0 1	0 0 1 0
0 0 1 1	0 0 1 0	0 1 1 0	0 0 1 1
0 1 0 0	0 1 1 0	0 1 1 1	0 1 0 0

0	1	0	1	0	1	1	1	1	0	0	0	1	0	1	1
0	1	1	0	0	1	0	1	1	0	0	1	1	1	0	0
0	1	1	1	0	1	0	0	1	0	1	0	1	1	0	1
1	0	0	0	1	1	0	0	1	0	1	1	1	1	1	0
1	0	0	1	1	1	0	1	1	1	0	0	1	1	1	1

其余部分对应结果  
为无关项略去

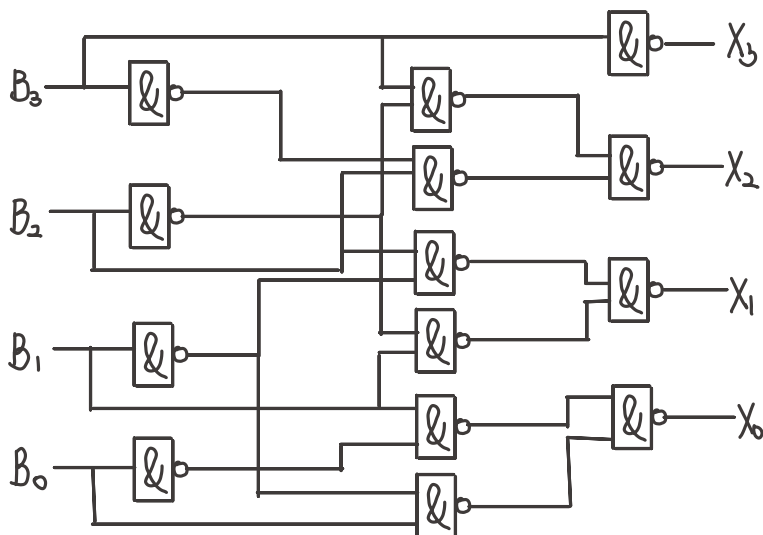
(1) 8421 BCD码转循环码

$$X_3 = B_3 \quad X_2 = \overline{\overline{B_3 B_2}} \quad X_1 = \overline{\overline{B_2 B_1}} \quad X_0 = \overline{\overline{B_1 B_0}}$$



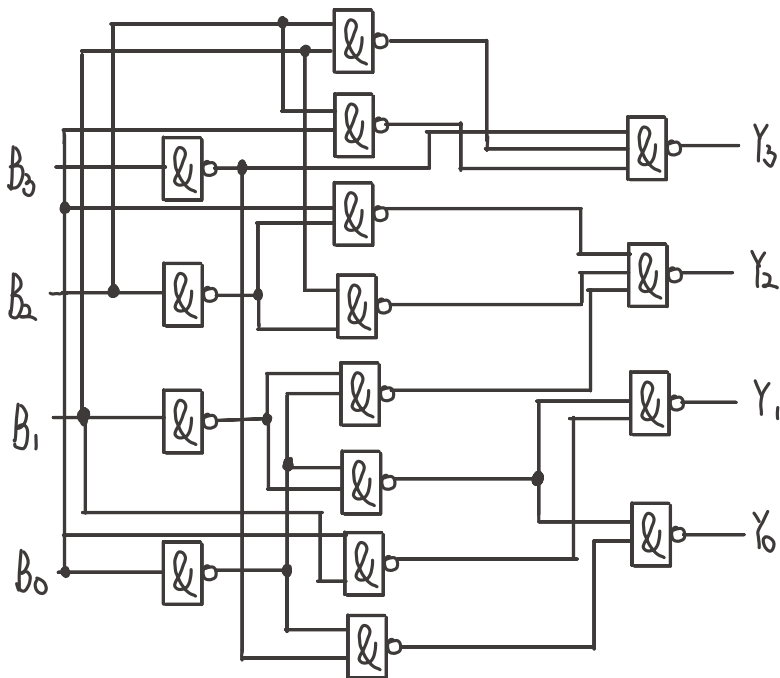(2) 8421 BCD码转余3码


$$Y_3 = \overline{\overline{B_3}} \quad Y_2 = \overline{\overline{B_2 B_0}} \quad Y_1 = \overline{\overline{B_1 B_0}} \quad Y_0 = \overline{\overline{B_2 B_1}} \quad Y_0 = \overline{\overline{B_2 B_1}} \quad Y_0 = \overline{\overline{B_2 B_1}}$$



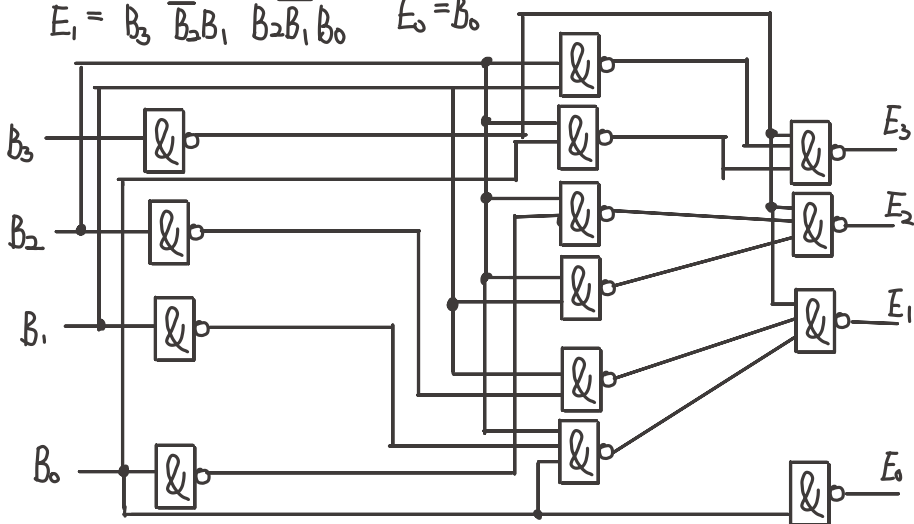(3) 8421 BCD 码转 2421 码

$$E_3 = \overline{B_3} \overline{B_2 B_0} \overline{B_2 B_1} \quad E_2 = \overline{B_3} \overline{B_2 B_0} + \overline{B_2 B_1}$$

$$E_1 = \overline{B_3} \overline{B_2 B_1} \overline{B_2 B_0 B_0} \quad E_0 = B_0$$



### 311 (1) 四变量表块：给定真值表


A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1

续表

1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

求逻辑表达式
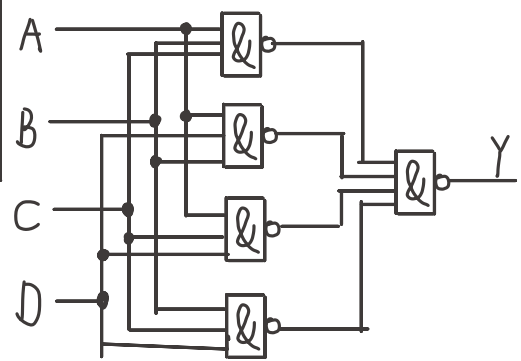
$$Y = \overline{BCD} \overline{ACD} \overline{ABD} \overline{ABC}$$




### (2) 偶检电路：真值表如下

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0

续表


1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

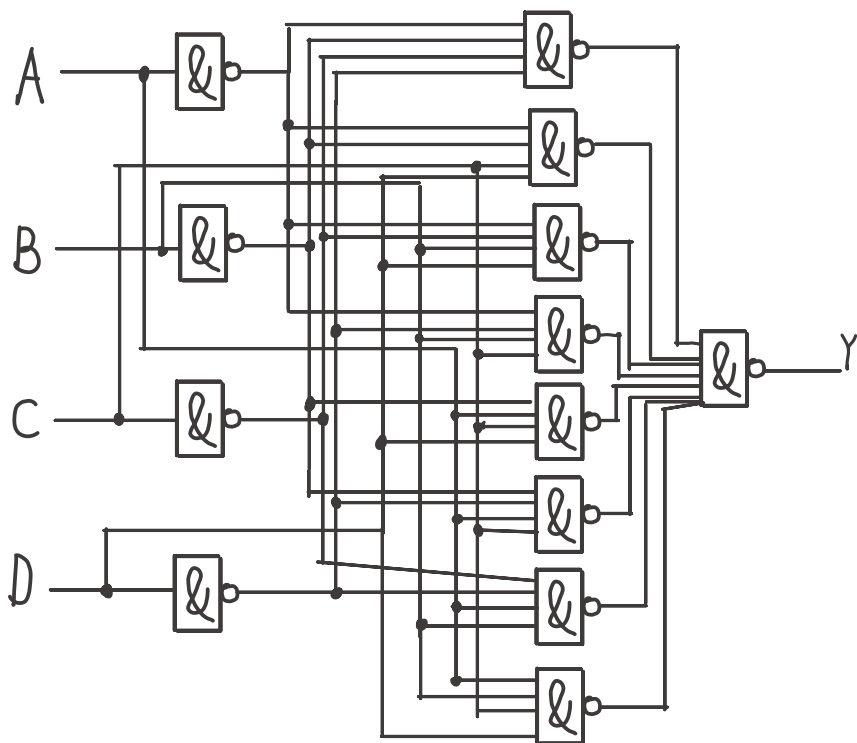逻辑表达式  $Y = \sum(m_0, m_3, m_5, m_6, m_9, m_{10}, m_{12}, m_{15})$




3/2

编码器

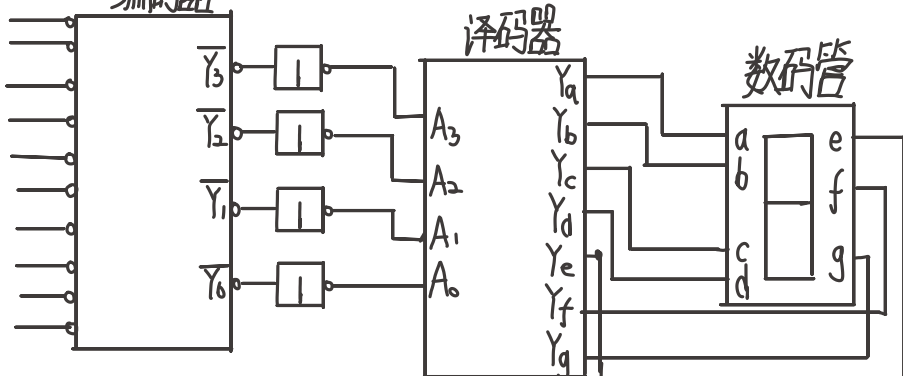

313

芯片 74153 简化结构如左图

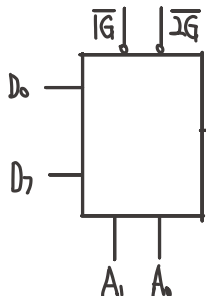

逻辑表达式 (当只使用 MUX1 时)


$$Y = A_1 A_0 D_3 + A_1 \bar{A}_0 D_2$$

$$\bar{A}_1 A_0 D_1 + \bar{A}_1 \bar{A}_0 D_0$$

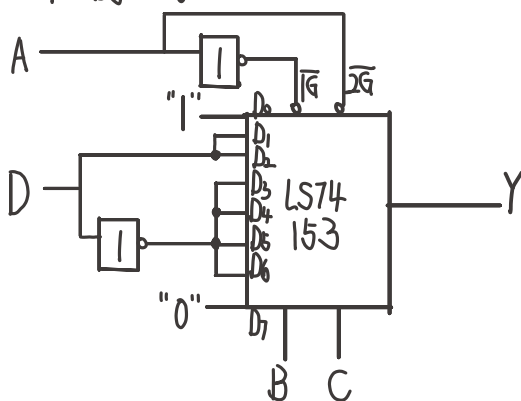(1)  $Y_1 = \sum_{ABCD} (m_0, m_1, m_3, m_5, m_6, m_8, m_{10}, m_{12})$  [需要使用两个 MUX 表达式和其它不同]

令  $\bar{I}_G = \bar{A}$ ,  $\bar{I}_{2G} = A$ ,  $A_1 = B$ ,  $A_0 = C$   $D_0 = 1$ ,  $D_1 = D_2 = D$

$D_3 = D_4 = D_5 = D_6 = \bar{D}$   $D_7 = 0$  电路图如下




(2)  $Y_2 = \sum_{ABCD} (m_0, m_2, m_4, m_5, m_6, m_7, m_8, m_9, m_{14}, m_{15})$

$ABCD = \bar{A}\bar{B}\bar{D} + \bar{A}B + \bar{A}\bar{B}C + ABC$

$A_1 = A$ ,  $A_0 = B$   $\bar{I}_G = 0$   $\bar{I}_{2G} = 1$

$D_0 = \bar{D}$   $D_1 = 1$   $D_2 = \bar{C}$   $D_3 = C$

电路图连接如左 (D4~D7 略)

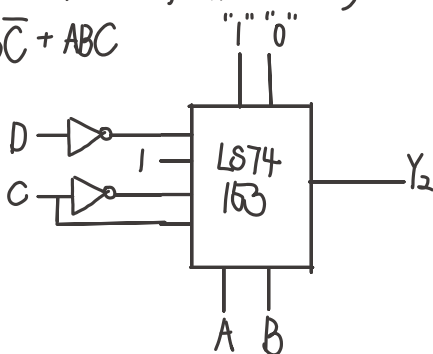


$$(3) Y_3 = \overline{A}B + B\overline{C} + C\overline{D} + D\overline{A} = \overline{C}\overline{D}(A+B) + C\overline{D} + \overline{C}D + CD\overline{A}B$$

$$\therefore A_1 = C \quad A_0 = D \quad D_0 = A+B \quad D_1 = D_2 = 1 \quad D_3 = \overline{A}B$$

$$\overline{1G} = 0 \quad \overline{2G} = 1$$

电路图如下  
(D<sub>4</sub>~D<sub>7</sub>略)

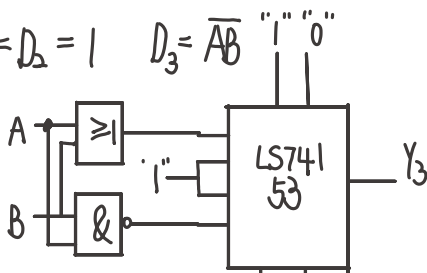


$$(4) Y_4 = BD + \overline{C}D + \overline{A}\overline{C} = BD\overline{C} + B\overline{D}\overline{A}\overline{C} + \overline{B}D\overline{C} + \overline{B}\overline{D}$$

$$\therefore A_1 = B \quad A_0 = D \quad \overline{1G} = 0 \quad \overline{2G} = 1$$

$$D_0 = 1 \quad D_1 = D_3 = \overline{C} \quad D_2 = \overline{A}\overline{C} = \overline{A+C}$$

(D<sub>4</sub>~D<sub>7</sub>略)

电路图如下

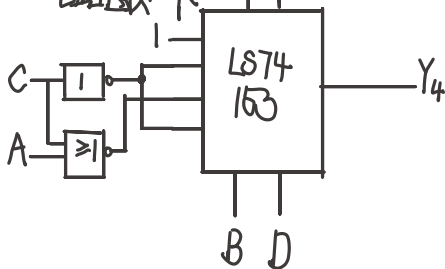


3.14 解 全加器表达式

$$S_1 = \sum m(1, 2, 4, 7) = \overline{Y_1} \overline{Y_2} \overline{Y_4} \overline{Y_7}$$

$$C_{1+1} = \sum m(3, 5, 6, 7) = \overline{Y_3} \overline{Y_5} \overline{Y_6} \overline{Y_7}$$

电路图如下

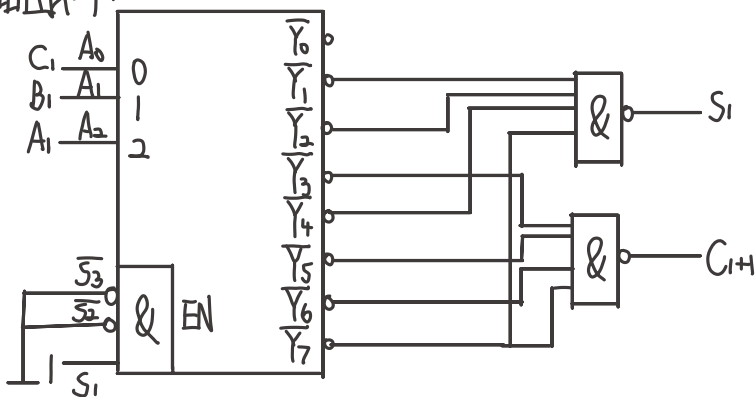


315 已知数据选择器输出逻辑函数

$$Y = \bar{A}_2 \bar{A}_1 \bar{A}_0 D_0 + \bar{A}_2 \bar{A}_1 A_0 D_1 + \bar{A}_2 A_1 \bar{A}_0 D_2 + \bar{A}_2 A_1 A_0 D_3 \\ + A_2 \bar{A}_1 \bar{A}_0 D_4 + A_2 \bar{A}_1 A_0 D_5 + A_2 A_1 \bar{A}_0 D_6 + A_2 A_1 A_0 D_7$$

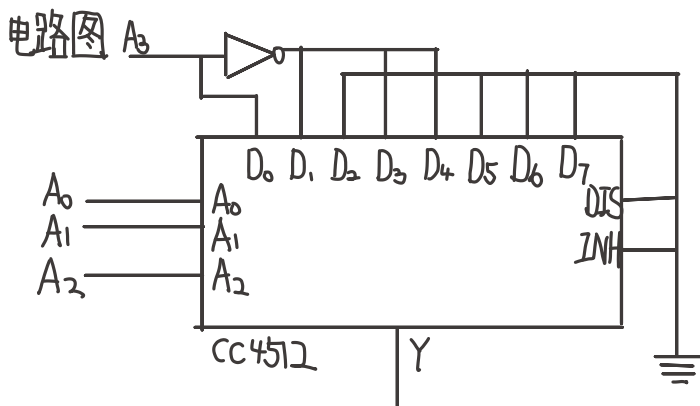(1) 已知  $Y_1 = \sum(m_1, m_3, m_4, m_8)$

$$= \bar{A}_3 \bar{A}_2 \bar{A}_1 A_0 + \bar{A}_3 \bar{A}_2 A_1 A_0 + \bar{A}_3 A_2 \bar{A}_1 \bar{A}_0 + A_3 \bar{A}_2 \bar{A}_1 \bar{A}_0$$

$$\therefore D_1 = D_3 = D_4 = \bar{A}_3 \quad D_0 = A_3 \quad D_2 = D_5 = D_6 = D_7 = 0$$



(2)  $Y_2 = \sum(m_0, m_1, m_3, m_5, m_6, m_7, m_{10}, m_{12}, m_{15})$

$$D_0 = D_3 = 1 \quad D_1 = D_2 = D_7 = A_0 \quad D_5 = D_6 = \bar{A}_0 \quad D_4 = 0$$

