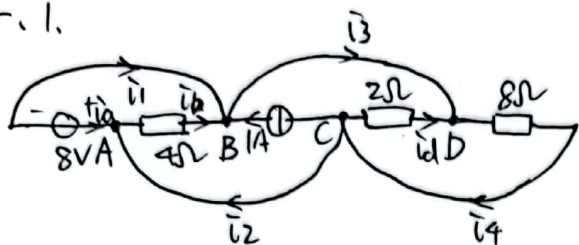


-1.

样卷1



由ABCD结点KCL有:


$$\begin{cases} i_1 + i_2 = i_5 \\ i_1 + i_5 + 1A = i_3 \\ i_4 = 1 + i_2 + i_5 \\ i_3 + i_5 = i_4 \end{cases}$$

由KVL有:

$$\begin{cases} 8 - 4i_5 = 0 \\ u_A = 2i_4 = 4i_5 \\ -8i_4 = 8 \end{cases} \Rightarrow \begin{cases} i_4 = -1A \\ i_5 = 2A \\ i_3 = 4A \end{cases}$$

(参考方向!)
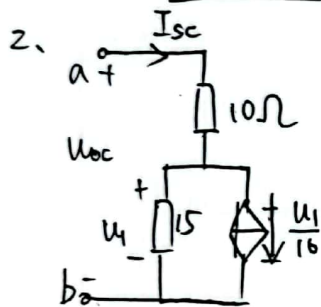
$$\therefore \begin{cases} i_1 = -8A \\ i_2 = -6A \\ i_3 = -5A \\ i_4 = -1A \end{cases}$$




$R_{eq} = \frac{u_{oc}}{I_{sc}}$ (等效电阻)

$$\therefore I_{sc} = \frac{u_1}{15} + \frac{u_1}{10} = \frac{u_1}{6}$$

$$u_{oc} = 10 I_{sc} + u_1 = \frac{8}{3} u_1$$
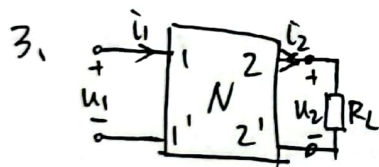
$$\therefore R_{eq} = \frac{\frac{8}{3} u_1}{\frac{u_1}{6}} = 16\Omega$$




$$\therefore \begin{cases} u_1 = 7i_1 - 3i_2 \\ u_2 = 3i_1 - 3i_2 \\ u_2 = i_2 R_L = 2i_2 \end{cases}$$

即: $i_2 = \frac{3}{5} i_1$

$$\therefore u_1 = 7i_1 - \frac{9}{5} i_1 = 5.2i_1$$

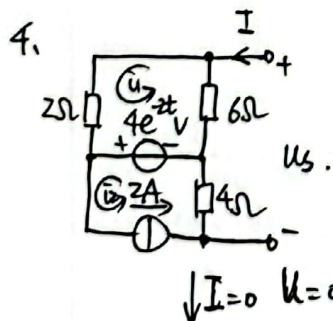
$$\therefore R_{in} = \frac{u_1}{i_1} = 5.2\Omega$$



回路1,2有: $\begin{cases} 4e^{-2t} + 8i_1 = 0 \\ i_2 = 2A \end{cases}$

$$\therefore u_3 = -6i_1 - 4i_2 = (3e^{-2t} - 8)V$$

$\downarrow I=0 \quad u=0$

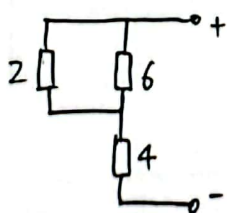


$$R_{eq} = 6 \parallel 2 + 4 = 5.5\Omega$$



扫描全能王 创建


5.

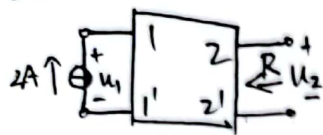

$$U = U_2 = 5V$$

$$R_{eq} = \frac{U_1}{I} = 5\Omega$$


6.

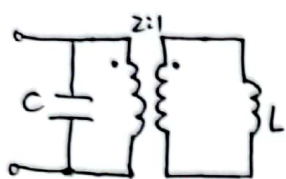

$$L_{eq} = 2^2 L = 4L$$

$$\therefore f = \frac{1}{2\pi\sqrt{L_{eq}C}} = 1000\text{Hz}$$

7.

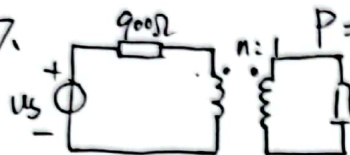


$$P = P_{max} \quad f_{00} = n^2 \times 16$$

$$\therefore n = \sqrt{\frac{900}{16}} = \frac{15}{2}$$

匝数比为 7.5.

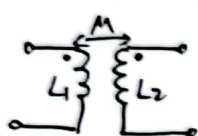8. 电感电压定义:

$$\begin{cases} \dot{U}_1 = j\omega L_1 \dot{I}_1 + j\omega M \dot{I}_2 \\ \dot{U}_2 = j\omega L_2 \dot{I}_2 + j\omega M \dot{I}_1 = 0 \quad (\dot{U}_2 = 0 \text{ 短路}) \end{cases}$$



$$\therefore \dot{I}_2 = -\frac{3}{4} \dot{I}_1$$

$$\therefore \dot{U}_1 = j\omega \dot{I}_1 \cdot \frac{15}{4}$$


$$\text{即: } L_{eq} = 3.75H$$

$$9. \quad \dot{i}_1 = I_{1m} \sin \omega t A \rightarrow \dot{I}_1 = \frac{I_{1m}}{\sqrt{2}} \angle -90^\circ$$


$$\dot{I}_1 = \dot{I}_2 + \dot{I}_A$$

$$\dot{i}_2 = 10\sqrt{2} \sin(\omega t + 30^\circ) A \rightarrow \dot{I}_2 = 10 \angle -60^\circ$$

即:

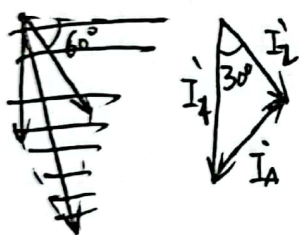

$$\therefore I_A = 10A$$

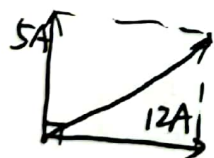10. C、L 相位相反, 均与 R 相差 90° , 有: $I_A = \sqrt{I_{A1}^2 + I_{A2}^2}$ 

$$= 13A$$

$$= 1) \quad U_1 = 10I_1$$

$$\begin{cases} -\frac{1}{20}U_1 + (\frac{1}{20} + \frac{1}{20})U_2 - \frac{1}{20}U_3 = 1 \\ -\frac{1}{40}U_1 - \frac{1}{20}U_2 + (\frac{1}{40} + \frac{1}{20} + \frac{1}{10})U_3 = \frac{20}{10} \\ U_3 = 20 - 10I_1 \end{cases}$$

$$\textcircled{1} \textcircled{2} \quad \textcircled{1} \textcircled{4} \rightarrow U_3 = 20 - U_1 \quad \textcircled{5}$$

$$\textcircled{2} \textcircled{3} \rightarrow 3U_3 - U_1 = 50 \quad \textcircled{6}$$

②

$$\textcircled{5} \textcircled{6} \rightarrow \begin{cases} U_1 = 2.5V \\ I_1 = 0.25A \\ U_2 = 20V \\ U_3 = 17.5V \end{cases}$$

③


④

$$\therefore U_A = U_2 + 10 \times 1A = 30V$$



扫描全能王 创建

三、该电路由两部分二端口网络级联：

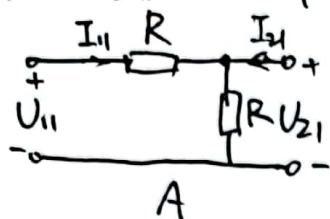

由A电路有：

$$\begin{cases} U_{11} = 2I_{11} + I_{21} \\ U_{21} = I_{11} + I_{21} \end{cases}$$

即：

$$\begin{cases} U_{11} = 2U_{21} - I_{21} \\ I_{11} = U_{21} - I_{21} \end{cases}$$

即：

$$T_A = \begin{pmatrix} 2 & 1 \\ 1 & 1 \end{pmatrix}$$

由B矩阵有：

$$\begin{cases} I_1 = 3U_2 \\ I_2 = 2U_1 - 4U_2 \end{cases}$$

即：

$$\begin{cases} U_1 = \frac{1}{2}I_2 + 2U_2 \\ I_1 = 3U_2 \end{cases}$$

即：

$$T_P = \begin{pmatrix} 2 & -\frac{1}{2} \\ 3 & 0 \end{pmatrix}$$

∴ 复合二端口矩阵 $T = T_A T_P = \begin{pmatrix} 2 & 1 \\ 1 & 1 \end{pmatrix} \begin{pmatrix} 2 & -\frac{1}{2} \\ 3 & 0 \end{pmatrix} = \begin{pmatrix} 7 & -1 \\ 5 & -\frac{1}{2} \end{pmatrix}$

四、(1) $U_S = \sqrt{12^2 + 15^2 + 16^2} = 25V$

(2) C、L 并联谐振频率： $\omega = \sqrt{\frac{1}{LC}} = 10^3 \text{ rad/s}$

~~C、L₂ 串联谐振频率~~


当 $\omega = 1000 \text{ rad/s}$ 时，其无法通过 C、L₁ 系统（发生谐振）

∴ $u_R(t) = 12 + 16\sqrt{2}\cos(2\omega t) V$

(3) $P = \frac{U_R^2}{R} = 12^2 + \left(\frac{16\sqrt{2}}{\sqrt{2}}\right)^2 = 400 W$

五、 $t < 0$ 时， $i(0_-) = 0 A$

$t > 0$ 时，列写回路方程（戴维宁）：

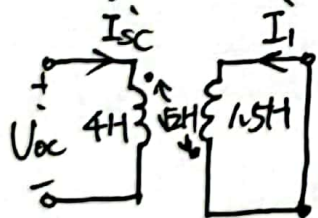

即：

$$\begin{cases} U_{oc} = -j\omega M I_1 + j\omega L_1 I_{sc} \\ 0 = j\omega L_2 I_1 + j\omega M I_{sc} \end{cases}$$

∴ $L_{eq} = \frac{U_{oc}}{j\omega I_{sc}} = \frac{8}{3} H$

∴ $\tau = \frac{L}{R} = \frac{2}{3} s$

∴ $i(\infty) = \frac{U}{R} = \frac{24}{4} A = 6 A$

∴ $i(t) = 6(1 - e^{-1.5t}) A, (t > 0)$

