

1. R 被加入电压 $P < 0$ N 功率为发出(产生) $\Rightarrow B$.

样卷3

2. 电压降: $U_a = \frac{R_1}{R_1 + R_2} U_s = 1V$

$U_b = \frac{R_3}{R_3 + R_4} U_s = 3V$

$\therefore U = U_a - U_b = 2V \Rightarrow D$

3. $3R_f \Rightarrow B$ (背的)

4. 理想电压源内阻为0. $\Rightarrow A$

5. 基波阻抗中虚部与频率有关: $Z_2 = (1 + j8)\Omega \Rightarrow D$

6. ~~$\frac{1}{R_1 + R_2} U_{a1} =$~~ 电流源串联电阻支路不被计算在方程中

故 $\frac{1}{R_1} U_{a1} = i_s - i \Rightarrow B$


7. 网孔电流法: $\begin{cases} 300I_1 - 200I_2 = 3 \\ -200I_1 + (200 + R)I_2 = -rI_1 \end{cases}$

$\therefore r = 100\Omega \Rightarrow A$


8. $i_1 = -4\cos(100t + 60^\circ)A = 4\sin(100t - 30^\circ)A$

$\therefore \Delta\varphi = -30^\circ - 60^\circ = -90^\circ \Rightarrow D$

9. 除 R_L 其余进行戴维宁变换, 短路电压源:

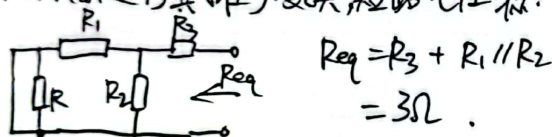

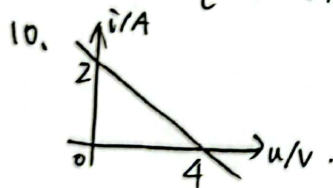
$\therefore R_L = R_{eq} = 3\Omega$ 时, $P = P_{max} \Rightarrow B$



有: $i = 2 - \frac{1}{2}u$
即: $u = 4 - 2i$

$\therefore \begin{cases} U_{oc} = 4V \\ R_{eq} = 2\Omega \text{ (方向*)} \end{cases}$

11. $i_L(0-) = 0A$

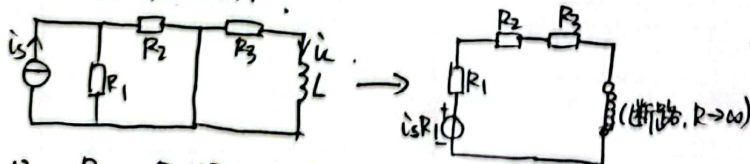

$\therefore u(0+) = i_s R_1 = 40V \Rightarrow D$

12. $R_{eq} = R_1 // R_2 = 5\Omega$

$U_{oc} = \frac{U_s}{2} = 10\sin(t)V$

$T = \frac{L}{R_{eq}} = 0.2s$


$i(0-) = 0A$
 $i(\infty) = \frac{U_s}{R_1} = 2A$

$\therefore i(t) = 2(1 - e^{-\frac{t}{0.2}})A \Rightarrow B$



扫描全能王 创建

13.

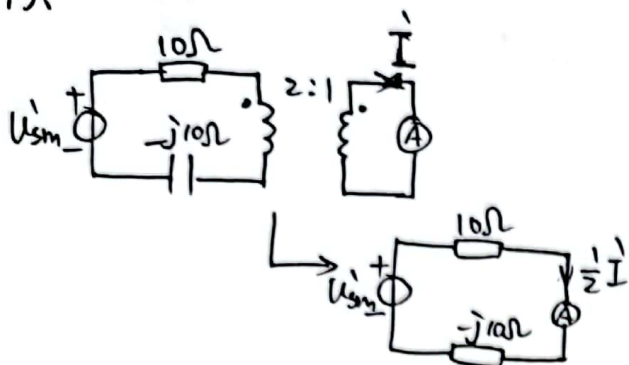

$$\therefore \frac{1}{2} \dot{I} = \frac{U_{sm}/\sqrt{2}}{10-j10}$$

$$\therefore \dot{I} = 2 \angle 45^\circ \text{ A}$$

$$\therefore I_A = 2 \text{ A} \Rightarrow A$$

14. $i(t) = \frac{1}{Z} \int u(t) dt$

$$= 5 \int 5 \sin 50t + 10 \sin 100t dt$$

$$= [0.5 \sin(50t - 90^\circ) + 0.5 \sin(100t - 90^\circ)] \text{ A} \Rightarrow A$$



15. $\dot{U}_2 = j\omega L_2 \dot{I}_2 + j\omega M \dot{I}_1$
 由于 $\dot{I}_1 = I_m \angle 0^\circ$ $\dot{I}_2 = 0$

$$\therefore \dot{U}_2 = -j\omega M I_m \angle 0^\circ = \omega M I_m \angle 90^\circ$$

$$\therefore u_2 = -\omega M I_m \cos \omega t \Rightarrow B$$

16. 线性电阻二端网络: $\frac{u}{i_s} = \frac{u'}{i_s'} \Rightarrow i_s' = 4i_s \Rightarrow D$

17.

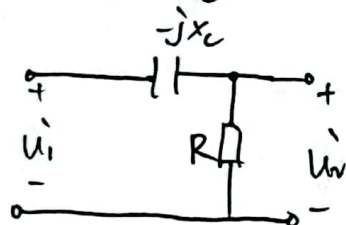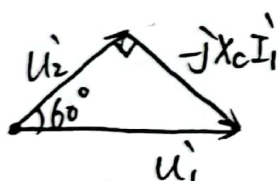


$$\therefore \frac{U_2}{U_1} = \frac{1}{2} \Rightarrow D$$

18. $I = \sqrt{4^2 + \frac{2.5^2}{2} + \frac{1.5^2}{2} + \frac{0.8^2}{2}} \text{ A} \Rightarrow C$
 ↑
 直流不需
 除√2

二、由 KVL 有: $-24 + 6i + i + 6 + i + 6 + 2i = 0$

$$\therefore i = 1.2 \text{ A}$$
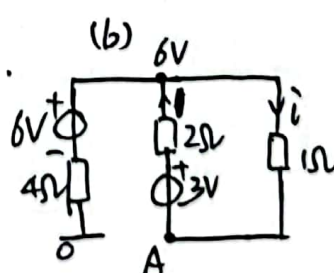
$$\therefore u_A = 6 + 7i - 24 = -9.6 \text{ V}$$




$$i = \frac{3}{1+2} = 1 \text{ A}$$

$$u_A = 6 - i = 5 \text{ V}$$



扫描全能王 创建


三、 $t < 0$ 时，有：

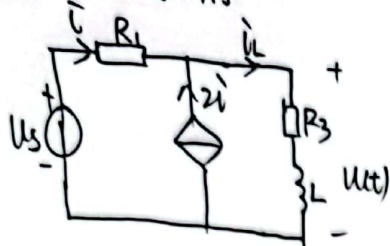

$$\begin{cases} i_L = 3i \\ U_s = iR_1 + i_L R_3 \end{cases}$$

$$\therefore i_L(0-) = 6A$$

$$U_L(0-) = 24V$$

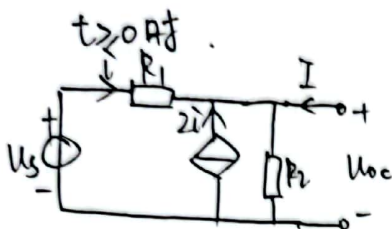

$$\text{KVP: } \begin{cases} 32 - iR_1 = U_{oc} \\ 2iR_2 + R_2(i + I) = U_{oc} \end{cases}$$

$$\therefore U_{oc} = 24 + I$$

$$\text{KVP: } \begin{cases} R_{eq} = 1 + R_3 = 5\Omega \\ U_{oc} = 24V \end{cases}$$


$$\therefore \tau = \frac{L}{R_{eq}} = 0.1s$$

$$i_L(\infty) = 4.8A$$

$$\therefore i_L(t) = (4.8 + 1.2e^{-10t})A$$

$$u_L(t) = i_L R_3 + L \frac{di_L}{dt} = (19.6 - 1.2e^{-10t})V$$

四、直接列方程：

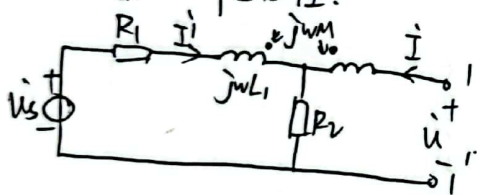


$$\begin{cases} U_s = I'R_1 + I'j\omega L_1 + I'j\omega M + (I' + I)R_2 \\ U = I'j\omega L_2 + I'j\omega M + (I' + I)R_2 \end{cases}$$

$$\therefore I' = \frac{60 - (j5 + 6)I}{12 + j10}$$

$$\therefore U = 30 + (3 + j7.5)I$$
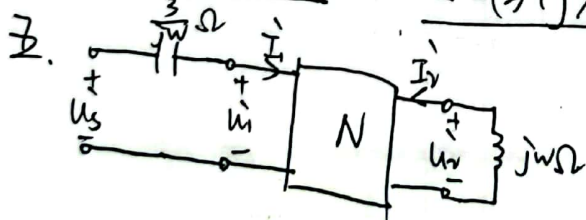
$$\text{即: } \underline{U = 30 \angle 0^\circ V}, \quad \underline{Z = (3 + j7.5)\Omega}$$



由Z矩阵有：

$$\begin{cases} U_1 = 7I_1 + 3I_2 \\ U_2 = 3I_1 + 3I_2 \end{cases}$$

由KVL有：

$$\begin{cases} U_s = I_1 \frac{3}{j\omega} + U_1 \\ U_2 = -j\omega I_2 \end{cases}$$

$$\therefore Z_{eq} = \frac{U_s}{I_1} = \frac{3}{j\omega} + 7 + \frac{9}{-3 - j\omega}$$

$$= 7 - \frac{27}{9 + \omega^2} + \left(\frac{j9\omega}{9 + \omega^2} - \frac{j3}{\omega} \right)$$

令 $\text{Im}[Z_{eq}] = 0$ ，有： $\frac{9\omega}{9 + \omega^2} = \frac{3}{\omega}$ 即： $\omega = \frac{3}{\sqrt{2}} \text{ rad/s}$

谐振频率为 $\omega = \frac{3}{\sqrt{2}} \text{ rad/s}$



扫描全能王 创建